

Design of FMCW Radar

Team Grildur Frostcrag

Charles Liu

Ghazanfar Alvi

Sandeep Banwait

Eugene Kim


Abstract

This paper presents the design and realization of a radar with the ultimate objective of providing range measurements. The system technology implemented is classified as frequency modulation continuous wave (FMCW) radar that can detect distances of targets and the speed of a moving object with relatively lower power. The size of the microwave radar system can be reduced by using higher frequencies. A 24 GHz radar design was considered but was disapproved of due to the increase losses associated with systems operating at such high frequencies. Therefore a 5.8 GHz system has been selected for the design which also has the advantages of having readily available components.

Introduction

The FMCW radar is composed of the RF and baseband subsystem. The RF system incorporates the RF subsystem and antenna. The baseband incorporates the gain stage and filtering of the down converted signal in preparation for sampling. The following block diagram depicts the basic layout of the coherent FMCW radar.

RF Subsystem Block Diagram

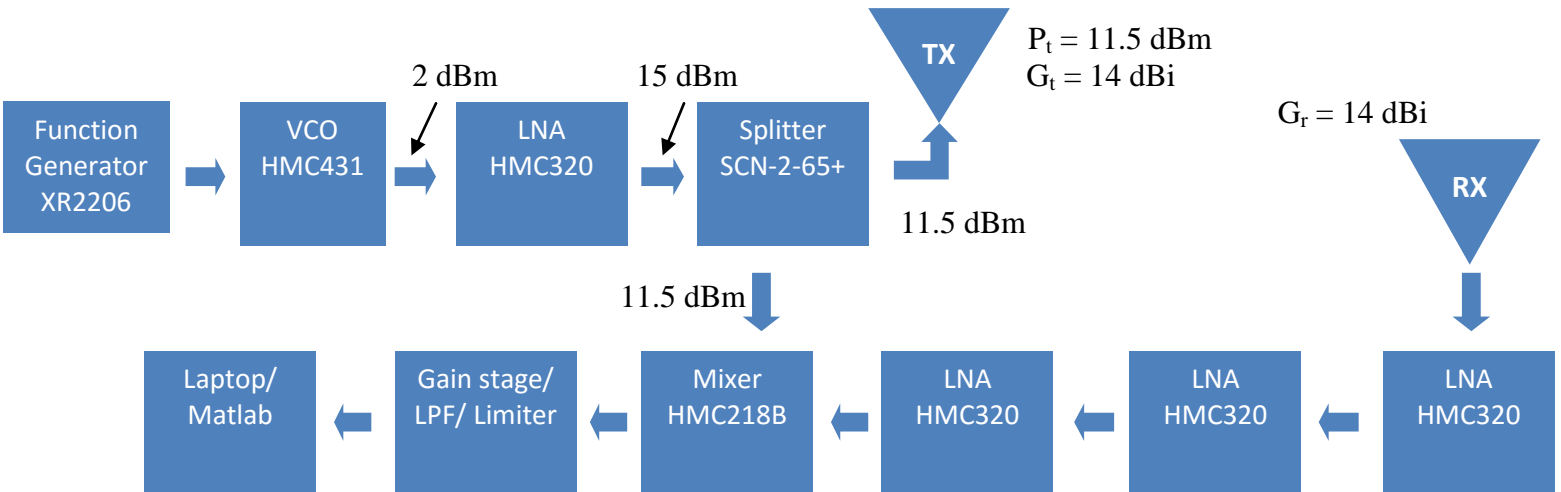

The proposed RF subsystem is bi static radar type which incorporates transmit and receive paths. It is implemented to increase the isolation between the two paths. The transmit path starts with the voltage controlled oscillator (HMC431) which is able to output a 2 dBm signal to sweep in the range of 5.6 to 6 GHz according to modulation voltage signal from the function generator. The swept signal is amplified by way of a low noise amplifier (HMC320) which provides a power amplification of 13 dBm at the operating frequency. After that the swept signal is divided by way of a splitter (SCN-2-6+) which introduces a 3.5 dBm insertion loss. A portion of the swept signal is coupled to the mixer as reference signal. The final transmitted power of the system is 11.5 dBm which is transmitted through a 14 dBi TX antenna. The received path starts with a series of low noise amplifiers. The required RF amplification at this stage will be

discussed later in this section. This amplified signal from the RX antenna is inputted to the mixer where it is down converted by mixing with the reference signal. This down converted signal is amplified at the gain stage and passed through low pass filter before it is sampled by the PC.

Once the transmit power of the radar is realized, Frii's equations is used to determine the received power. The goal is to design the receiver to detect a 0.3 meter squared target ranging at distances between 5 to 50 meters.

$$P_r = \frac{P_t G_t \sigma G_r \lambda^2}{(4\pi R^2)^2 4\pi}$$

With an operating frequency of 5.8 GHz the power received ranges from -52.4 dBm to -92.4 dBm for target ranges from 5 to 50 meters. To reduce the amount of amplification required at the baseband gain stage, RF amplification is implemented at the RF receiver path with a cascade of three low noise amplifiers (HMC320) with each providing a power amplification of 13 dBm at a noise figure of 2.5 dBm.

To characterize the receiver path of the RF subsystem Analog Devices provides ADIsimRF to calculated total gain, noise figure, signal to noise ratio and peak to peak output voltage. The calculations for receiver path for targets at 5 and 50 meters are shown below.


ADIsimRF receiver path calculation for target at 5 meters

The screenshot shows the ADIsimRF software interface. The main window displays a block diagram of the receiver path with four stages: Stage 1, Stage 2, Stage 3, and Stage 4. Stage 1, 2, and 3 are Low Noise Amplifiers (LNA), and Stage 4 is a Mixer (Mx). Below the diagram is a table of parameters for each stage and overall system performance.

	Stage 1	Stage 2	Stage 3	Stage 4
Receive	LNA	LNA	LNA	Mixer (Mx)
Toggle Tx/Rx	Temp Part	Temp Part	Temp Part	Temp Part
Input Freq (MHz)	5800	5800	5800	5800
Zin (Ohms)	50	50	50	50
Zout (Ohms)	50	50	50	50
Power Gain (dB)	13	13	13	-7
Voltage Gain (dB)	13	13	13	-7
IIP3 (dBm)	10	10	10	100
IP1dB (dBm)	17	17	17	91
Pin (dBm)	-52.4	-39.4	-26.4	-13.4
Pin Backoff (dB)	63.4	56.4	43.4	104.4
Peak Backoff (dB)	63.4	56.4	43.4	104.4
Noise Figure (dB)	2.5	2.5	2.5	0
Voltage (V)	3	3	3	0
Current (mA)	40	40	40	0

Input	Analysis	Noise Figure	Other Parameters
Number of Stages: 4	Output Power (rms): -20.4 dBm	2.6 dB	OIP3 (Po/2 per tone): 15.78 dBm
Input Power: -52.4 dBm	Output Voltage (rms): 21.35 mVrms	Output NSD: -139.2 dBm/Hz	IIP3 (Pin/2 per tone): -16.2 dBm
Analysis Bandwidth: 1 MHz	Output Voltage (pp): 60.33 mVpp	Output NSD: 24.5 nV/rtHz	IMD (Pin/2 per tone): -78.4 dB
PEP-to-RMS Ratio: 0 dB	OIP1dB: 21.78 dBm	Output Noise Floor: -79.2 dBm	SFDR: 63.3 dB
P1dB Backoff Warning: 10 dB	IP1dB: -9.2 dBm	SNR: 58.8 dB	ACLR (est.): -59 dB
Peak Backoff Warning: 1 dB	Power Gain: 32 dB	Input Rx Sensitivity: -101.2 dBm	Pwr Consumption: 0.36 W
Min S/N for Demod: 10 dB	Voltage Gain: 32 dB		

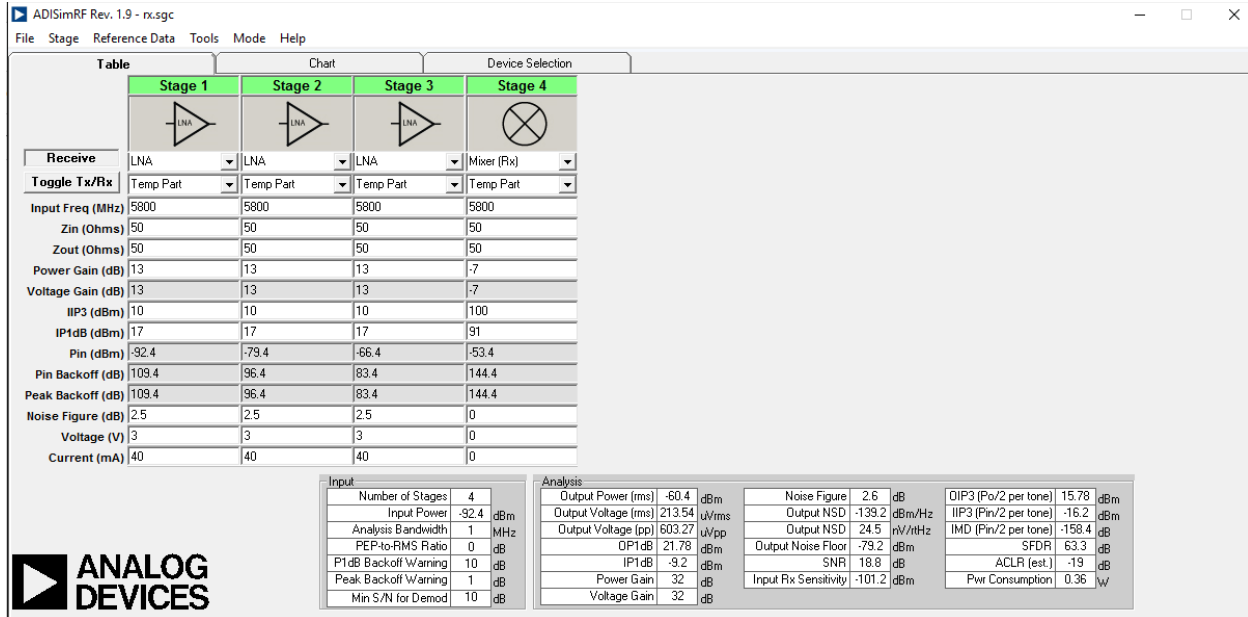ADIsimRF receiver path calculation for target at 50 meters



The baseband circuit is designed to amplify the incoming signal and filter any noise received from the IF frequency of the RF circuit. The link budget table below summarizes the power received, mixer power output and mixer output voltage for targets at 5 and 50 meters. From this the gain required at the gain stage can be determined.

Range	Power Received	Mixer Power Output	Mixer Voltage Output
5m	-52.4 dBm	-20.4 dBm	60.3 mVpp
50m	-92.4 dBm	-60.4 dBm	603 uVpp

For weak signals detected at target ranges as far as 50m, amplification is required for the built in ADC of the PC's microphone to detect noticeable measurements. For the ADC of the microphone a minimum 25mV peak to peak signal was determined to be sufficient. To detect targets at the maximum range of 50 meters, amplification provided by the gain stage should be x40. Any signal higher than 1.2 volts peak to peak would be limited by the limiter circuit.

Component Selection

This section will cover the process involved in selecting components that meet system design specifications detailed in the previous section. The selection process has been divided into RF components and baseband components. The table below summarizes the main components selected in this process.


Device	Model	Manufacturer	Specification
Function Generator	XR-2206CP	Exar/Jameco	Frequency Range: 0.01-1MHz

			I = 14 mA
Voltage Controlled Oscillator	HMC431LP4ETR	Analog Devices	Power Output: 2dBm Vcc = 3V I = 33mA
Power Splitter	SCN-2-65+	Mini-Circuits	Insertion loss: 3.5 dBm Passive
Low Noise Amplifier (13 dBm)	HMC320MS8GE	Analog Devices	Noise Figure: 2.5 dBm Power Gain: 13 dBm I = 40 mA
Mixer	HMC218BMS8GE	Analog Devices	Conversion Loss: 7 dBm LO Power: + 13 dBm Passive
Antenna	5.8GHz 4-Patch Array	Ripafire	Gain = 14 dBi Bandwidth: 350 MHz Range: 5.6 – 5.95 GHz
Gain Stage Amplifier	TL972IP	Texas Instruments	
Active Low Pass Filter	MAX291CPA+	Maxim Integrated	Corner Frequency Range: 0.1 Hz - 25 kHz


HMC431LP4ETR Voltage Controlled Oscillator:

The Voltage Controlled Oscillator (VCO) generates the RF signal transmitted by the radar. The VCO requires many considerations when selecting. For range measurements applications an optimal VCO would have a tuned voltage to oscillate linearly in conjunction to a linear output in the frequency of operation. Constant power output over this range would be ideal. In addition the VCO should have low phase noise. The VCO chosen for the design was the HMC431LP4ETR manufactured by Analog Devices. The graphs below, taken into account for the analysis, are obtained from the datasheet provided by Analog Devices. The expected operating frequency is between 5.6 to 5.95 GHz. To operating in this range the tuning voltage would span between 2 to 6 volts. Based on the sensitivity vs. tuning voltage graph in this range there is a deviation of 50 MHz/Volt. Although this is not perfectly linear it is acceptable for radar applications. The output power remains constant at just above 2 dBm for the entire frequency range.

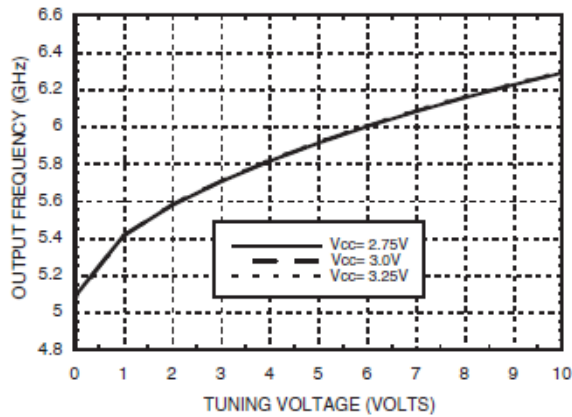
Frequency vs. Tuning Voltage, $T = 25^{\circ}\text{C}$



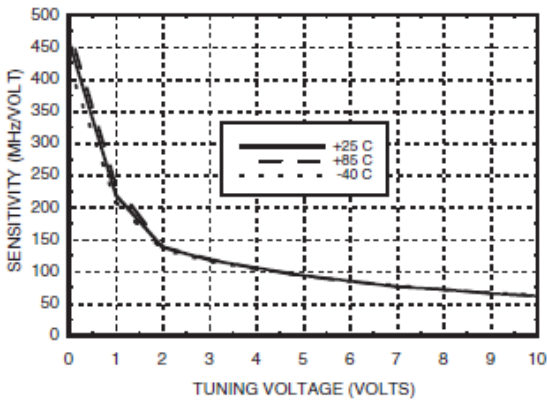
Sensitivity vs. Tuning Voltage, $V_{cc} = +3\text{V}$



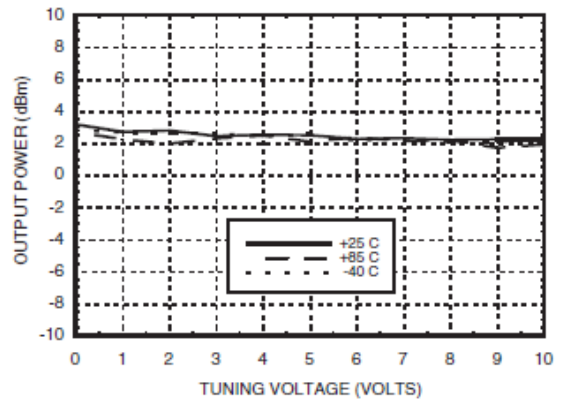
Output Power vs. Tuning Voltage, $V_{cc} = +3\text{V}$



Phase Noise vs. Tuning Voltage

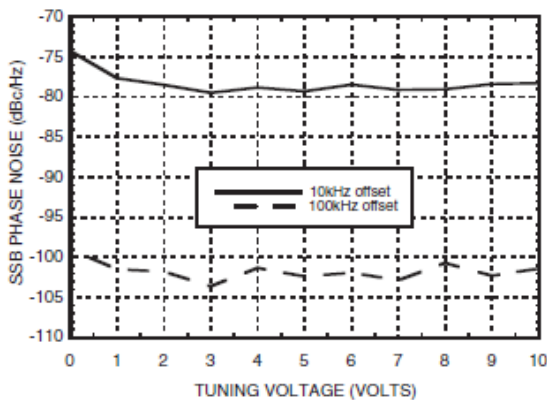

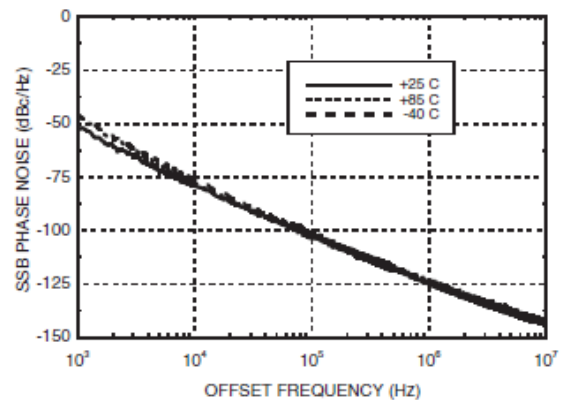Typical SSB Phase Noise @ $V_{tune} = +5\text{V}$




XR-2206CP Function Generator:

Once a VCO has been selected a function generator must be taken into account. Initially the Teensy 3.1 in conjunction with the MCP4921 DAC was taken into consideration but due to size and power constraints another option was chosen. The XR-2206CP is a monolithic function generator Exar that is able to produce the required triangle waveform to drive the VCO without a microcontroller and digital to analog converter.


HMC320MS8GE Low Noise Amplifier:

The Low Noise Amplifier (LNA) is required before the splitter and the RF input of the mixer to allow for enough amplification of the signal entering the baseband circuit. When selecting a LNA, it is critical to choose one that provides high power amplification and relatively low noise figure which would reduce the signal to noise ratio introduced during cascading of multiple LNAs. Also an LNA that does not require a complicated bias network would simplify the assembly process. The HMC320MS8GE by Analog Devices was chosen for the radar design which provides the option for configuration with three bias conditions. The graphs below are obtained from the datasheet. To maximize power amplification of each LNA, a high power bias is chosen.

Gain @ Three Bias Conditions

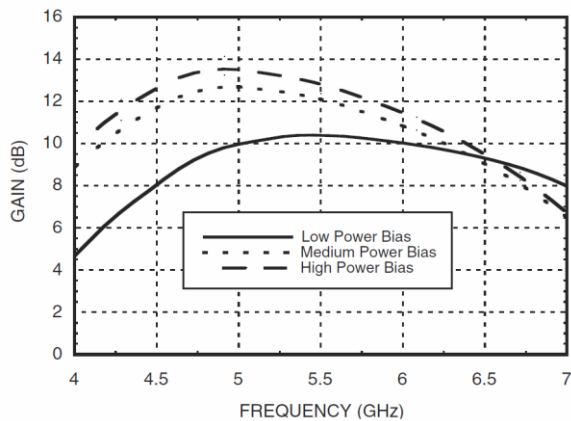

Noise Figure @ Three Bias Conditions

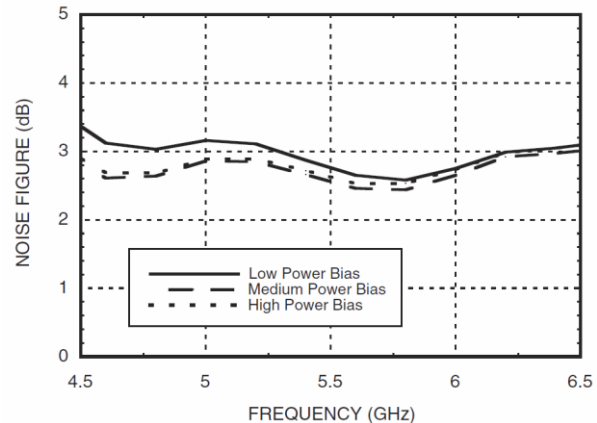

SCN-2-65+ Power Splitter

When selecting a power splitter it is important to pay close attention to insertion losses and a number of other key factors. The selection of the SCN-2-65+ Power Splitter by Mini-Circuits is justified in the following table. For a frequency range for 5500-6500MHz the insertion loss remains low between 3.5 and 3.8 dB. The splitter can provide a large isolation of about 17 dB which is good. Also the splitter had the added benefit of easy soldering and being low on cost.


Electrical Specifications

FREQUENCY (MHz)	INSERTION LOSS (dB) ABOVE 3.0 dB		ISOLATION (dB)		PHASE UNBALANCE (Degrees)		AMPLITUDE UNBALANCE (dB)		RETURN LOSS (dB)	
	Typ.	Max.	Typ.	Min.	Typ.	Max.	Typ.	Max.	INPUT Typ.	OUTPUT Typ.
5500-6500	0.8	1.1	17	11	3	5	0.1	0.4	18	16
5700-5900	0.5	1.0	17	11	2	4	0.1	0.3	22	16

HMC218BMS8GE Mixer

The ideal mixer would be a double balanced mixer which has the advantages of good port isolation, noise protection and linearity. Fortunately Analog Devices provides the HMC218BMS8GE that meets these specifications in a passive double balanced topology. The graph below shows the conversion loss for a given LO drive of the mixer. With an expected LO drive of about +11dBm for our system design, the conversion loss remains constant at 6.5 dBm under the expected operating frequencies.

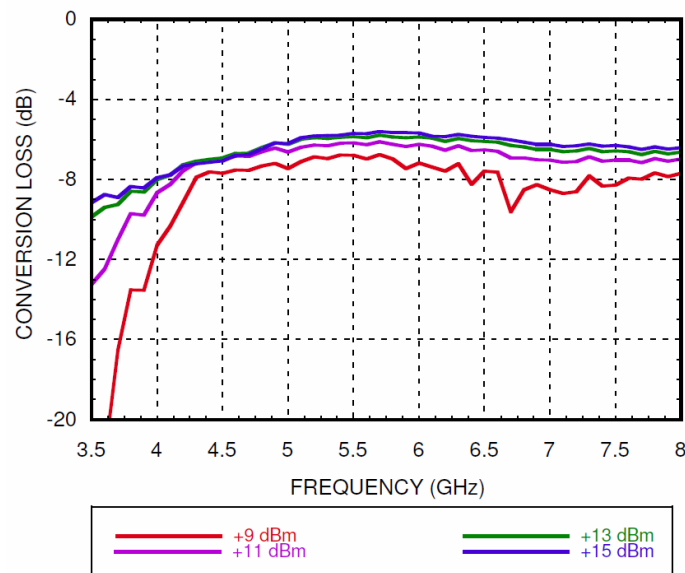Conversion Loss vs. LO Drive **RFIN = -10 dBm, LSB**



TL972IP Amplifier (Gain Stage) and MAX291CPA+ (Low Pass Filter)


The gain stage and active low pass filter in consideration is a modified version from the baseband design implemented in lab 1 for the quarter 1 radar which had a cut off frequency of 15 kHz. Modifications include the cascading of 2 amplifiers (TL972IP) in the gain stage to achieve the required amplification of x40 and an improved dedicated active lowpass filter IC (MAX291CPA+) which can provide a maximally flat passband response as a 8th order Butterworth filter.

Design Schematics and Printed Circuit Board Designs

A Printed Circuit Board (PCB) is a board made up of a set of pads and copper interconnects that connect at various points to create a proper circuit. PCBs are made up of a substrate (usually fiberglass), copper wirings, soldermask, and silkscreens all stacked up in layers to achieve a compact design. The use of PCB simplifies the wiring process, reduces error caused by wiring, and decreases the overall size and weight of the device. The absence of messy wires gives us cleaner runs and user-placed test pins allow for fast and easy debugging. For our project, we used KiCAD to design the schematics and PCB layouts of our PCBs. KiCAD is not only free, but straightforward in the way that it simplifies the conversion from schematic to PCB layout design. Another option would be to use EAGLE, but the fact that its free version is not for commercial use makes it less appealing to KiCAD.


Schematics

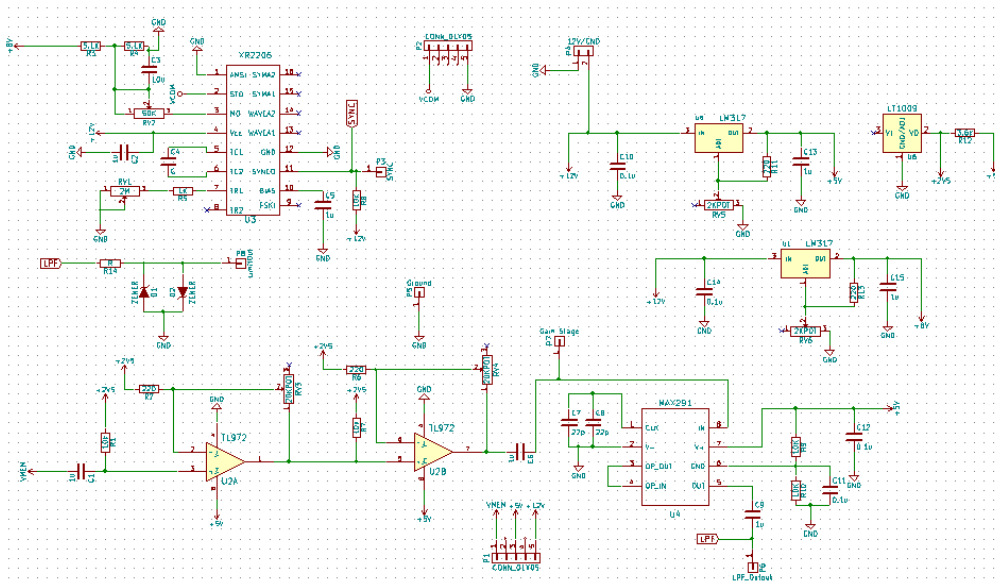In order to start making your schematic you need to finalize your parts. Once that is done, you can start inputting the parts into the schematic. A schematic is a simplified diagram that is visually easy to comprehend compared to the




mess that is the PCB layout. By making connection in the schematic, we can convert it using KiCAD so that it will automatically make the connections apparent for us when we are at the PCB layout stage. That is why it is crucial not to make a mistake in wiring for schematic design as it will lead to guaranteed failure with the PCB. To make a schematic design, you place your component symbols onto the page and connect the available pins to each other. You have the option to create your own symbols and have various tools such as voltage sources, ground pins, pin connectors, etc. that simplify the process. Above you can see the schematic design of the baseband from our project.

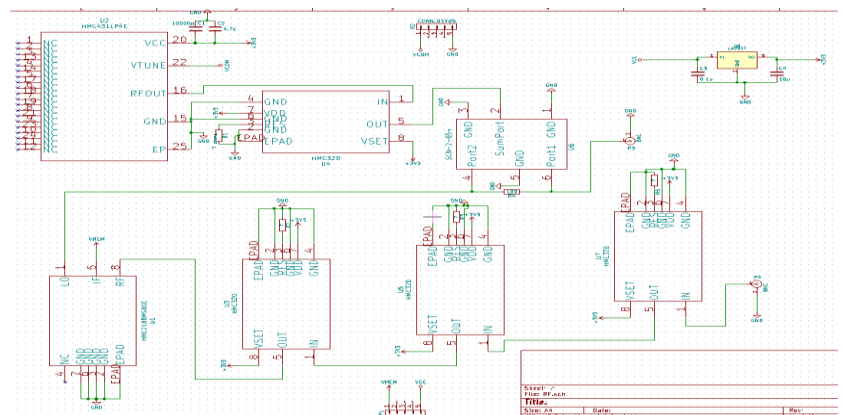Take note that each component has a name and value. This is to help



differentiate the components once they are placed on the board. For our circuit U2A and U2B are the same component, but if they were two different, yet similar components then the part's label would be very important to avoid mismatching. On the right is the RF schematic for our radar.


Footnote Design

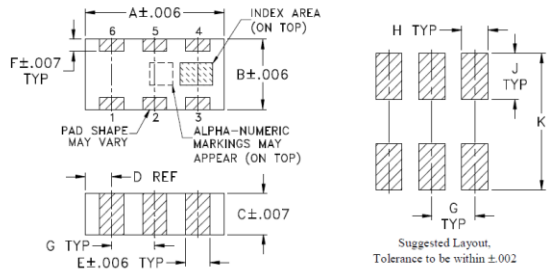

CASE #	A	B	C	D	E	F	G	H	J	K	L	M	N	P	WT GRAM
FV1206-1	.126 (3.20)	.063 (1.60)	.035 (0.89)	.024 (0.61)	.022 (0.56)	.011 (0.28)	.039 (0.99)	.024 (0.61)	.042 (1.07)	.123 (3.12)	--	--	--	--	.020

don't supply them so we have to make them on our own. To make your own footprint, you use KiCAD and your component's datasheet to look at the dimensions of your part so that you can space out the soldermask layer correctly.

The figure shown above is a company's provided instructions on proper footnotes for the component that we purchased from them. Notice how detailed all the dimensions are and how they have some values that give us more leeway with plus/minus values, making it easier for us to create a proper footprint. On the right is our completed version of the same footprint provided shown in KiCAD's Footprint Editor. The red squares are the parts of the board that will be connected to the copper interconnects.

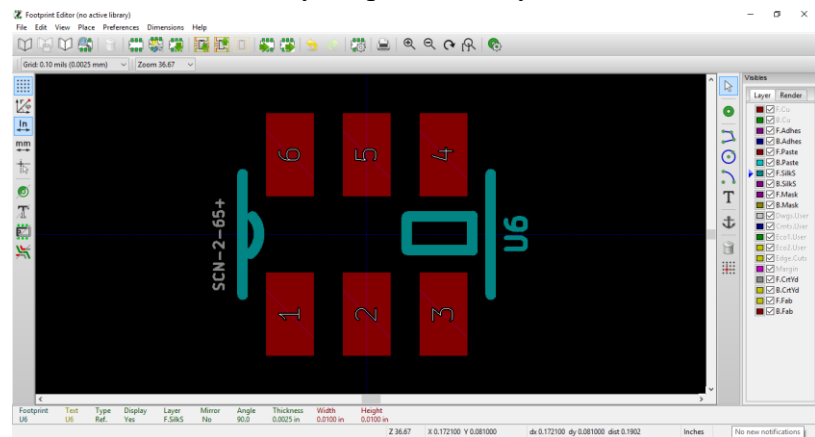


PCB Layout Design

The next step is where we generate the actual layout of our PCB. Using KiCAD, we can specify how we want the area of our PCB by making an outline of the borders. Generally you want to create one that is rectangular for portability and cleanliness. KiCAD automatically converts your premade schematics and supplies all the components onto your PCB layout for easy designing. The key to PCB layout design is to organize your components in a way that will minimize distance from paths to avoid messy connections and decrease overall size of the board.

Once you have decided on where you want your components you need to connect them by placing traces in between them. Since KiCAD generated all the components from your translated schematic, when you trace the components together there will be lines that show where to

connect each part. This is really convenient because without this tool you would need to manually check with the schematic to make sure of where you should be connecting and that would take too much time. You can place a trace on either the front or back copper layer and connect them together by using a via. This simplifies the process when there are too many connections already on one side giving us more space to connect. It is ideal to only use one layer, but it is not realistic for circuits that have many components especially when trying to decrease board size. Make sure not to place the vias directly on the pins of the components, this will cause improper connections. Another thing to point out is to be cautious of trace length and width. The longer the length the greater the dissipation of power so we aim for shorter length to give more power to the circuit. Same goes for width where we want thicker traces, however this is harder to do when trying to minimize board area since larger trace width means less space to connect with. Another important note is that trace connections should avoid making sharp ninety degree turns. These result in issues due to manufacturers not being able to etch it properly.

Below you can see one of our finished Baseband PCB layouts. Notice that there are two colors for traces. The red means that it is on the top copper layer and the green means it is on the bottom. We made it so that all of our components will all be on the top layer so in order to connect resistors and capacitors you must place the traces on the top layer. However for parts such as the potentiometers (RV1-6) which have in hole connections, you can use either the top or bottom since they are connected in both layers.

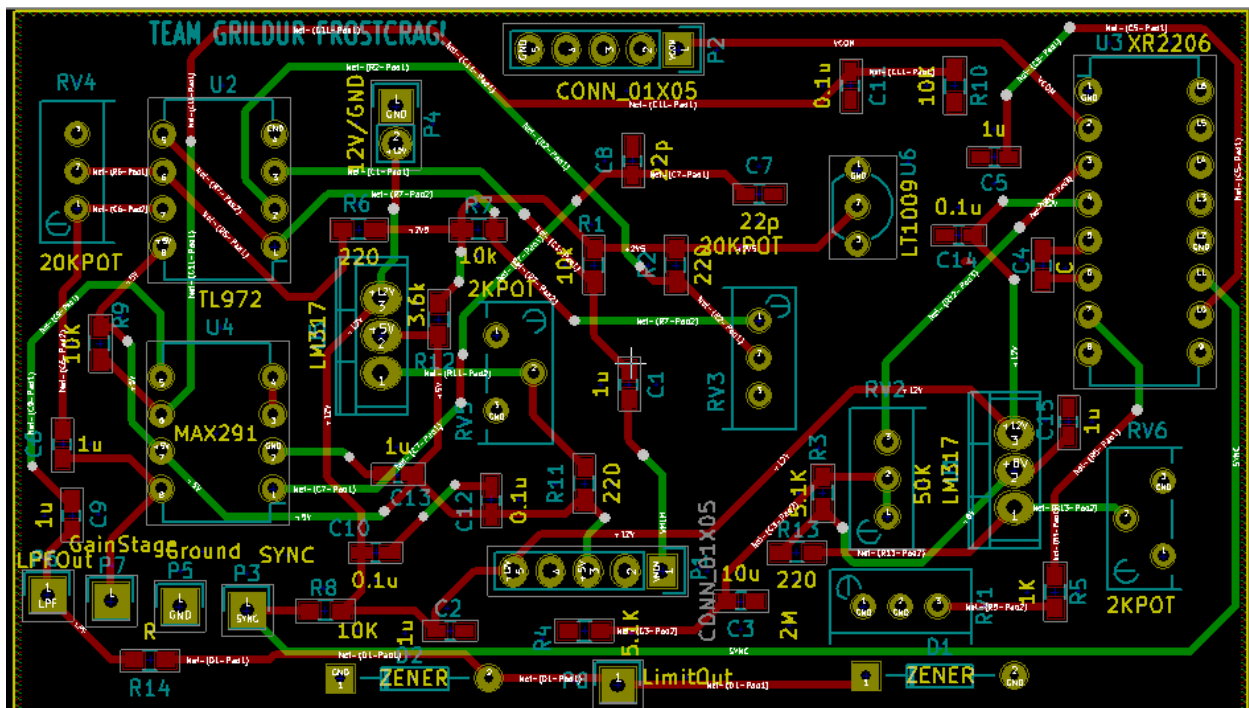


Another thing to mention is to notice the green square shaped components lined up in the left hand corner. Those are test pins that we placed to simplify input and output connections while making debugging less chaotic. We mentioned in an earlier section that PCB design makes


debugging easier and it is the capabilities that test pins give us that allow for clean and simple debugging of our circuit.

RF PCB Layout

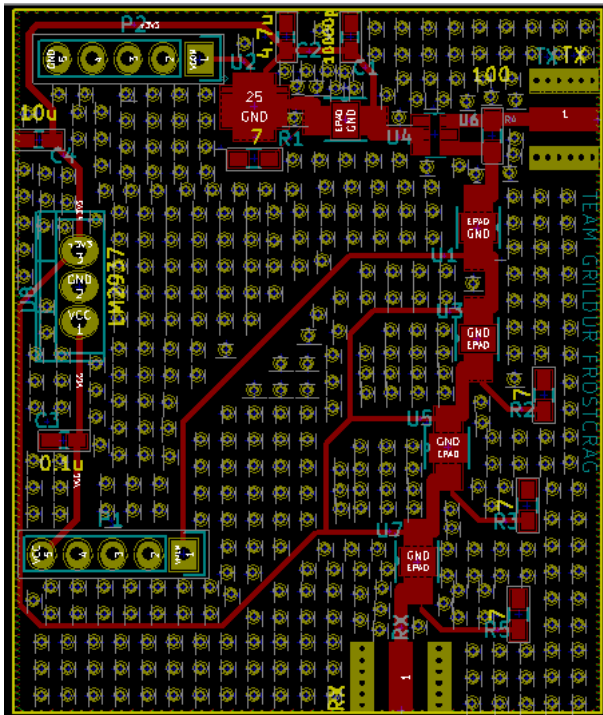Because of the high frequencies used for RF circuits we must take note of the traces. The transmission lines must not be perpendicular to each other and should remain as straight as possible because turns can cause a 180 degree phase dissonance causing the signal to weaken or cancel. Notice that there are two paths so they may look like they are going ninety degrees but they are separate paths.



In the figure on the left is one of our finished RF PCB layouts. As you can see there are numerous amount of vias scattered around the PCB. The vias are necessary around the transmission line in order to prevent RF signals from resonating onto the ground plane and stops the generation of noise. Using a web app called Wcalc we were able to find the parameters needed to make accurate transmission line width and spacing. As shown in the picture below, by inputting our fixed 6.15 mil spacing parameter we were able to get our transmission line width which is 37.5 mil.

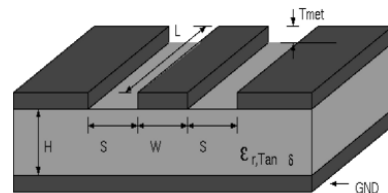

Metal width (W)	37.6913	mil	calc
Metal spacing (S)	6.15	mil	calc
Trace length (L)	142.802	mil	
Metal thickness (Tmet)	0.8	mil	
Metal resistivity (RHO)	5e-08	Ohm	- m
Metal surface roughness (RGH)	0.001	mil	-rms
Substrate thickness (H)	62	mil	calc
Substrate relative dielectric constant (Er)	4.8		calc
Substrate loss tangent (tand)	0.01		
Frequency	5.8	GHz	
<input type="checkbox"/> Analyze	<input type="checkbox"/> Reset	<input checked="" type="checkbox"/>	Include bottom side ground
Characteristic Impedance	50	[ohms]	
Electrical Length	43.4184	[degrees]	

Printed Circuit Board Assemblies

Soldering, using fusible metal alloy as an adhesive, played a key role in constructing the quarter two RF radars. It is imperative that soldering is done correctly, otherwise, one erroneous connection can make the difference between a working and non-working system, potentially causing time consuming troubleshooting and frustration. The components previously prototyped on a bread board in quarter one, are now compacted into different shaped integrated circuits and passive components that lie in the realms of millimeters; with each different shaped component, there are several techniques and tools that can ensure a proper connection.

Safety Concerns

Before soldering, it is **HIGHLY** recommended to put on goggles. While soldering, bits of solder may fly out and if you're looking closely at the board, which tends to happen while soldering the smaller passive components, melted bits of solder, upon contact, can cause permanent damage to the eyes. Also, there may be cases where a peer may accidentally bump into you, causing the solder tip to jerk towards you're face. Although these cases may seem very situational, you may prevent these permanent consequences with simple eyewear.

The soldering iron is typically 600 to 750 degrees fahrenheit, so please be aware of where you each whenever you grab the iron as well as your surroundings. Quickly turning while holding the iron, may come into brief contact with a peer who the user isn't aware of, however this brief contact is more than enough to cause serious burns. Also when soldering a wire you may find it quickly heats up, so it is advised to hold the wires with tweezers or clamps to avoid burns.

It is also advised to work with constant ventilation: near a window, or have a fan running that may direct the solder fumes away from the solderer. The most common types of solder is a lead-tin alloy with a rosin core, which cause fumes that is known to cause occupational asthma and dermatitis. If ventilation isn't possible, you may want to consider investing in a face mask.

Finally, as mentioned above, the most common type of solder is has strong concentration of lead which is a known neurotoxin. Lead can pose significant chronic health effects with digestive problems, memory, and reproductive problems [1]. Although lead is harmless upon direct skin contact, problems arise when dust from lead remains on the solderer's hands which can be ingested when eating, smoking, biting nails, etc, so it is highly suggested to wash your hands after each soldering session.

Different methods

There are three main methods that were utilized for constructing our radar: Hot Iron, Hot plate, and Hot Air. Hot Iron is analogous to a heated pen, which can melt solder at precise locations, and clean up existing connections. Hot plate uses, as the name implies, a hot plate where a printed circuit board (PCB) may sit on top on, and conduct enough heat to melt solder on the surface. Finally, Hot air is essentially a blow dryer, that typically operates in the range of 275 - 400 degrees Fahrenheit



ahrenheit, and is primarily for specific connections and aligning existing connections.

Figure 1. Hot Iron, Hot Plate, Hot Air.

Hot Iron

Hot iron was the primary method in constructing our PCBs. Because the Hot Iron is only heating a specific part of the PCB and the Iron can be simply lifted off the PCB if damage is a concern, I found it to be the safest method of construction. Hot Iron works well with smaller components such as resistors and capacitors, but it cannot be used for IC components that have a grounded pad. If there are different tips available, typically the more finer the tip, you will have better accuracy and control of applied the solder. Before soldering, I would clean the iron of any excess solder by heating it up, and scraping it with steel wool. Also if the iron looks dull, I would apply some solder onto the tip, and clean it until it looks shiny. If the iron looks dull, it may transfer heat slower, so cleaning it after each use is advised.

To begin, I will go over soldering potentiometers, pin headers, and other pin based PCB components. Before soldering, have the components in place into the PCB positioned as you intend them to stay in. Have the hot iron in your dominant hand, and the solder wire in the other. Soldering from the bottom side of the vi, first place the soldering iron onto the vi, and then apply

solder to the tip of the iron, where it's in contact with the vi. After applying solder, remove the iron first, and keep the component in place for a second or so to let the solder harden. Once one pin is in place, it is unlikely that the rest will move from place, so you may quickly solder the other pins without being concerned with holding the rest of the pins in place.

Moving on, I will discuss how to solder resistors and capacitors. Put the tip of the iron in contact with the copper pad, then quickly dab the solder wire at the tip. Due to the nature of the solder, it will reposition itself on the copper, so you do not need to be concerned with solder positioned outside the footprint. Once you have successfully applied solder onto one side of an interconnect, grab your passive components with a sharp-tipped tweezers. Make sure to level your passive component as flat as possible with the PCB to ensure a strong connection and to prevent tombing. Once you have leveled your passive component, heat the solder previously applied, then slide the passive component into place. Remove the iron first then the tweezers. Hold the component in place with tweezers, and after a second or so, the solder should be hardened and the component should be in place. To finish the connection, apply solder onto the other side of the component.

*Note, you do not need a large amount of solder for a sufficient connection; very little solder is needed for a proper connection. An indication of an appropriate amount of solder is to look for a "heel" shape connection, but for those who are unsure, a small ball of solder connection is more than enough. The capacitor on the left has two small balls of solder for its connection while the resistor, the left side in particular, has a "heel" shape connection.

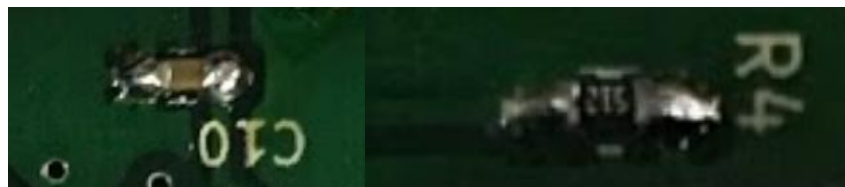


Figure 2. Different types of proper connections.

Hot Plate

As shown in figure 1, the hot plate is a very simple device. Simply set the setting of by turning the knob, and the light shown on the front-left side of the device indicates whether or not the plate is active. The hot plate works well with soldering IC components, especially ones with a grounded connection underneath the component pad. With the hot plate, you will be using solder flux which is a gray paste in a syringe that has a lower melting point than traditional solder. Be warned, if the PCB is left on the plate for too long, it can easily damage the board, so you must

work quickly once it's in use.

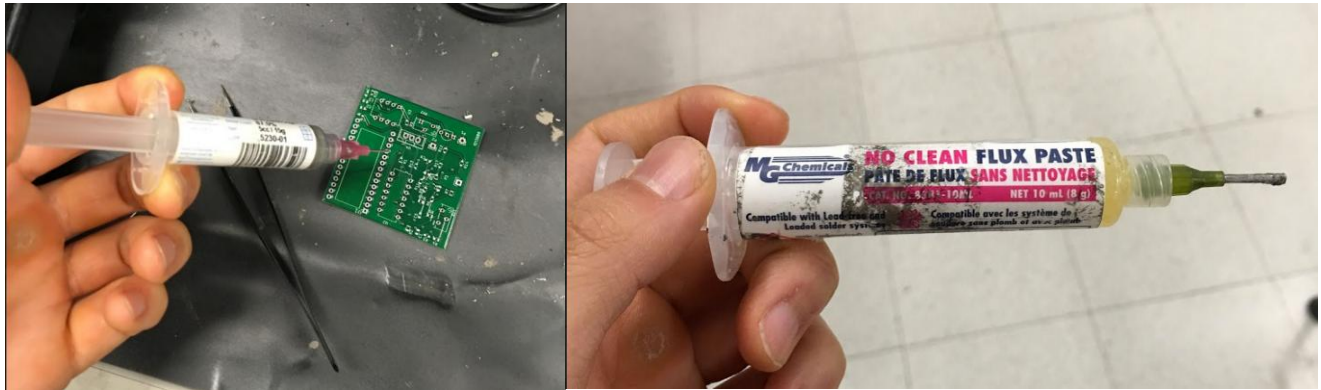


Figure 3.

To begin, apply a small amount of paste onto the all the connection sites you intend to use the hot plate for. It is better to set all your IC's in as few runs as possible because with each run, there is a higher risk of damaging the PCB with every trial. Set the hot plate onto low, or around 230F, and place the PCB onto the pad. The paste will quickly melt and look just like traditionally melted solder. Once the paste as melted, quickly place your components on top of the melted solder. To know if there is a good connection, tap the components to the side very lightly and the solder should snap the IC back into place. Once all the components are placed properly, carefully move the PCB off the plate. From my experience, solder paste solidifies much slower than rosen core solder, so be wary of components moved from place, and solidifying improperly. Also, do not try to move a hot plated pcb with your bare hands; it will be extremely hot. Also we wary with the amount of solder paste applied: if to much solder is applied, IC legs may become shorted with one another and establish connections that lead to failure.

Hot Air

Shown in figure, the hot air is also another simple device. Once lifted off it's stand, it will begin heating up, and once its placed back into the stand, it will automatically shut itself off. I typically operated the hot air at 270C, which is hot enough to melt both types of solders. Hot Air is a great tool to realign solder components, and could also be a tool to form connections as well. Before applying hot air onto the solder, I always make sure to apply drops of flux where i'm going to air to help with the conduction and to remove impurities at the solder connection site. Also, if you make solder connections on all the connection sites of your component, for an example both sides of a resistor, then you can rely on hot air to properly align them. In figure 4, the PCB is shown before applying hot air, and is evidently unpolished. However if there is solder at each connection footprint, the hot air will snap each component into place. This greatly speeds

up the soldering process because if there is a sufficient connection, you can simply hot air it later to refine it, instead of attempting to perfectly align every component when its initially soldered on.

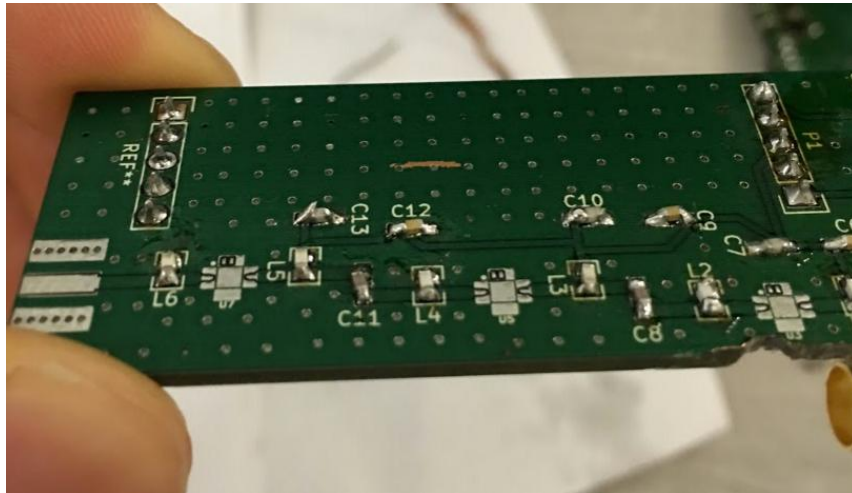


Figure 4. PCB before hot airing.

Mentioned before, you could also use the hot air to place components. Placing soldering paste on the PCB just like the hot plate, the hot air can be operated to melt the soldering paste, but doing minimal damage to the PCB. This was a alternative I utilized frequently over the hot plate, because it takes much more time for the hot air to damage the board, and also I may focus the heat in the specific location I'm soldering, minimizing interference with other solder components and damage to the PCB.



Final tips

If there was excess solder applied, I would use two main methods: scraping, and soldering wick. In cases where the component has several adjacent connections, like the VCO and LNA IC components, you could clean the iron, and gently hold the tip of the iron where the excess solder is, or scrap it away from the connection. By bringing a cleaned solder iron to a connection, a bit of the melted solder will attach itself to the iron, which may be enough to clear a unwanted short. If there is a great excess however, this method doesn't work, so you may turn to the soldering wick. To use the wick, place a strip on top of the area with an excess amount of solder. Then press down on the wick with the hot iron, and hold it in place until the wick stick absorbs the solder. Note that the wick does heat up, so you may want to hold the strip of wick in place with tweezers. In the case of removing through hole components, you may heat on side, while pulling the component out until all the solder in contact is melted. Heat transfer in solder goes relatively quick, but if it takes to long for the heat to travel to the other side of the pin, you could also apply

two soldering irons on each side, while a second person pulls on the component until it frees. Once you remove a pinhole component, there are times where excess solder remains in the vi, which may block any future components going in. To remove this solder, you could use the wick, or another tool called the soldering tube. It acts as a vacuum, and sucks in any melted solder. First you would heat one side of the vi, and then place the opening of the tube as flat as possible on the other. Once the solder melts, you release the spring in tube, the black button in figure 5, and it will suck the solder up.

Antenna Choice

Antennas that operate in the 5.8 GHz frequency range are readily available as they are commonly used in UAV applications. The antenna of choice is the 4-patch array antenna by Ripafire which is specified with an antenna gain of 14 dBi and frequency range of 5.6 - 5.95 GHz. Below is the S11 return loss characteristics of the antenna obtained from a network analyzer. The antennas perform as expected.

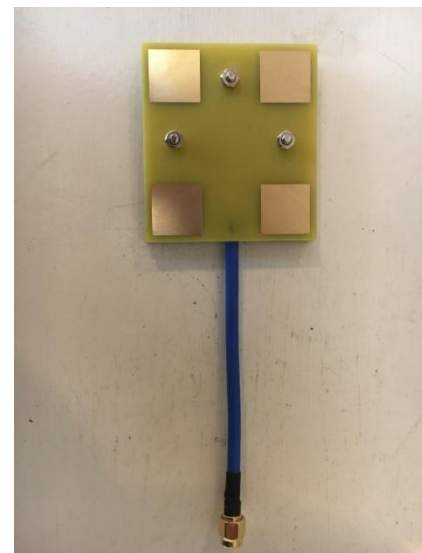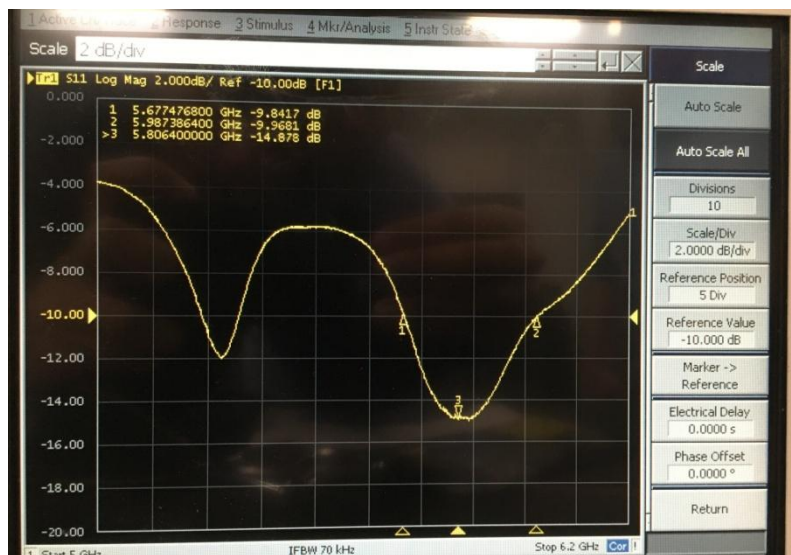

Testing and Results

First we had to make sure that the 5.8 GHz antenna we were going to use with our circuit, were fully functional. Checking it on network analyzer we found out our antenna (Fig 1) has a bandwidth of 350MHz as measured from S11 return loss, shown in Fig 2.

The function generator XR2206 was tested to make sure it was giving the triangular wave function with $V_{avg} = 4.1V$ (Fig 3). After soldering all the parts on the baseband board, we started changing the values of potentiometers to get the required values; from 2V to 6V.

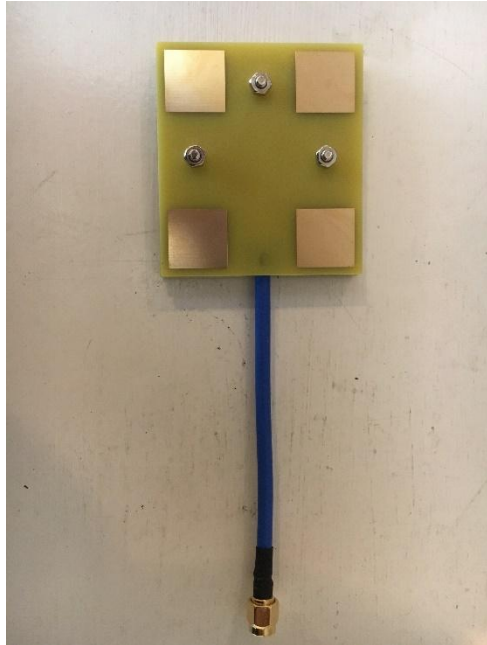


Fig 1: 5.8 GHz antenna. The screws are to hold the three plates of antenna together

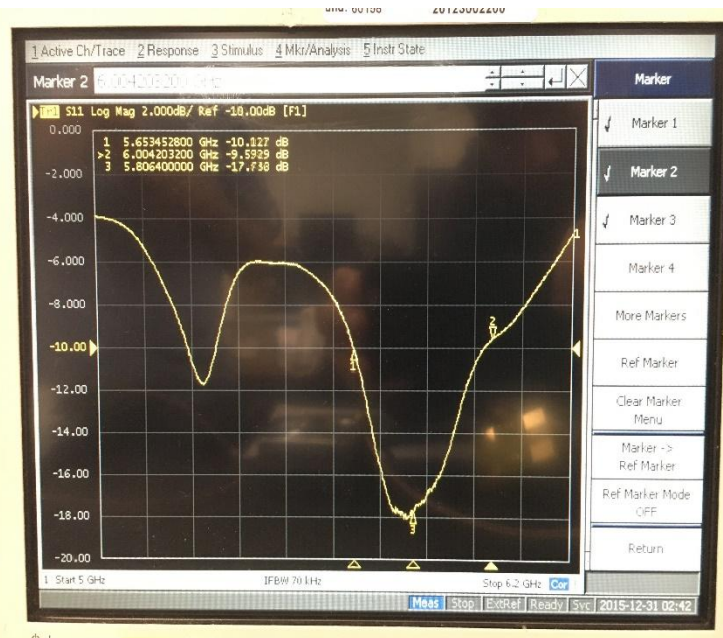


Fig 2: Results of 5.8 GHz antenna on network analyzer

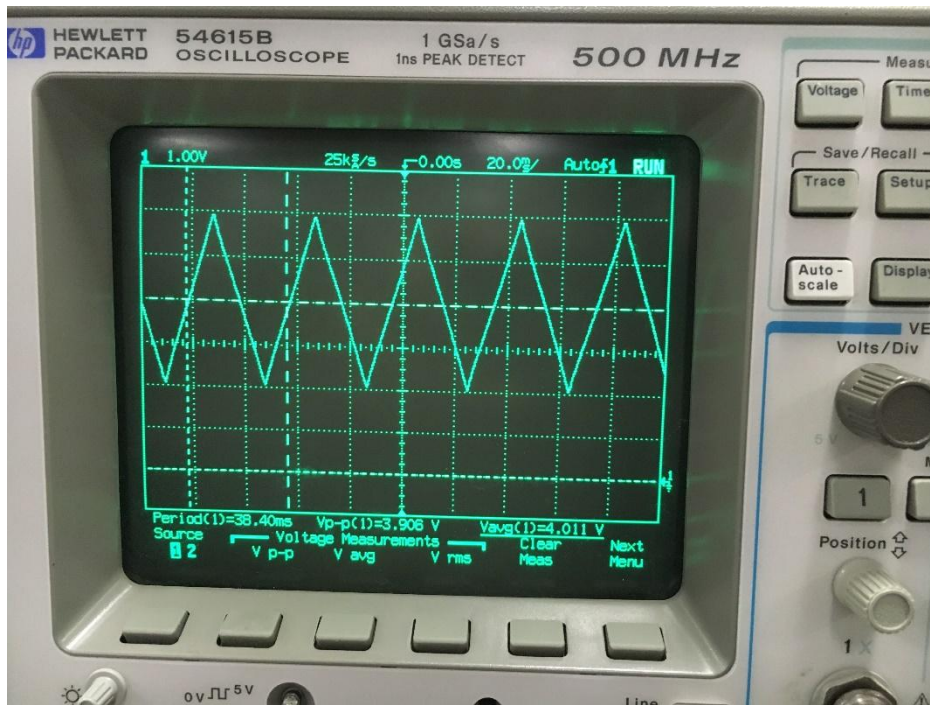


Fig 3: Triangular wave from a functioning XR 2206

While changing the values on the Potentiometers, we were also making sure that the sine wave on the oscilloscope does not get distorted or clipped. We were expecting a power amplification of 100 from our baseband but at the end we were getting a maximum amplification of roughly 20.6, which surely wasn't enough. (Fig 4)

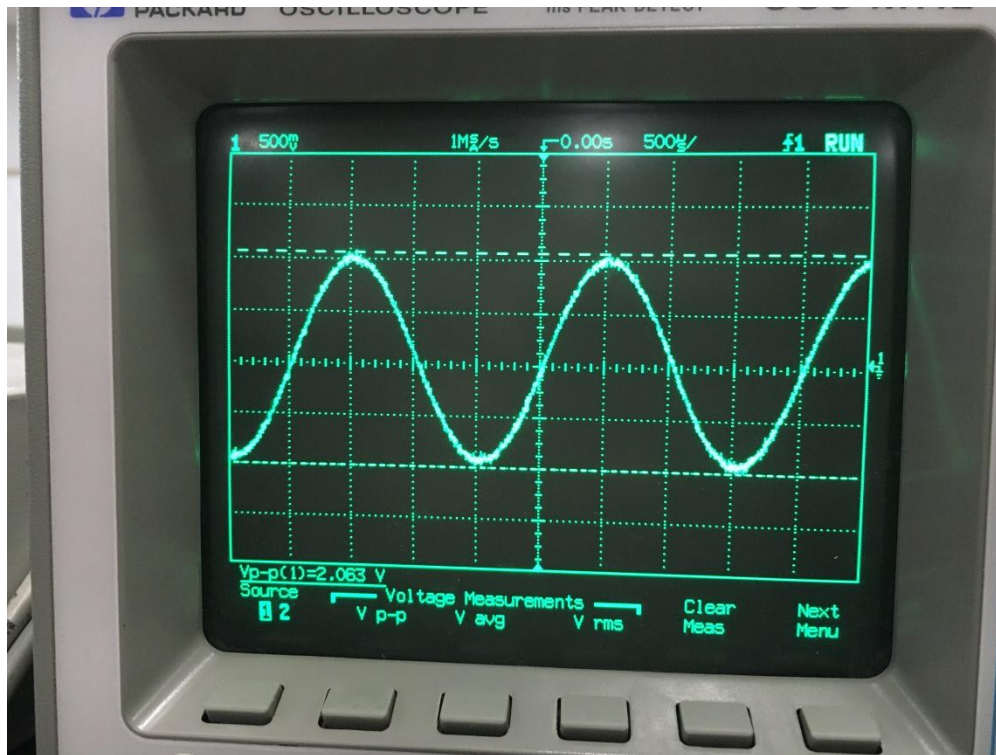


Fig 4: Input $V_{PP} = 0.1V$ and output $V_{PP} = 2.063$, giving amplification of 20.6

We decided to build a prototype of the circuit on the breadboard giving it the ideal conditions such as using different power sources for all the different values of voltages we required. Sure enough it gave the perfect results with the amplification depending on the V_{DD} of the amplifier. This helped us to easily get the amplification of 100. We started removing ideal conditions and used LM317 to produce 2.5V from 5V. The problem was persisting, although we were able to get a bit higher amplification of 25 now. There we learned that our resistors are maxing out and we have to change the 50k POT for 2M POT. After making the change we were able to get a amplification of 45.6, which was roughly half of our expected value but almost double of what we were getting before (Fig 5). After consulting with a few fellow students and doing some research we found out that one gain stage works just as good as two gain stages when it comes to amplification and rather helps with the noise too. We decided to start our experimentation with baseband board as is.

We, then, moved to our RF board and for the sake of simplicity, I will call the boards as B13 and B20 referencing to the amplification value of the majority of the LNAs on the

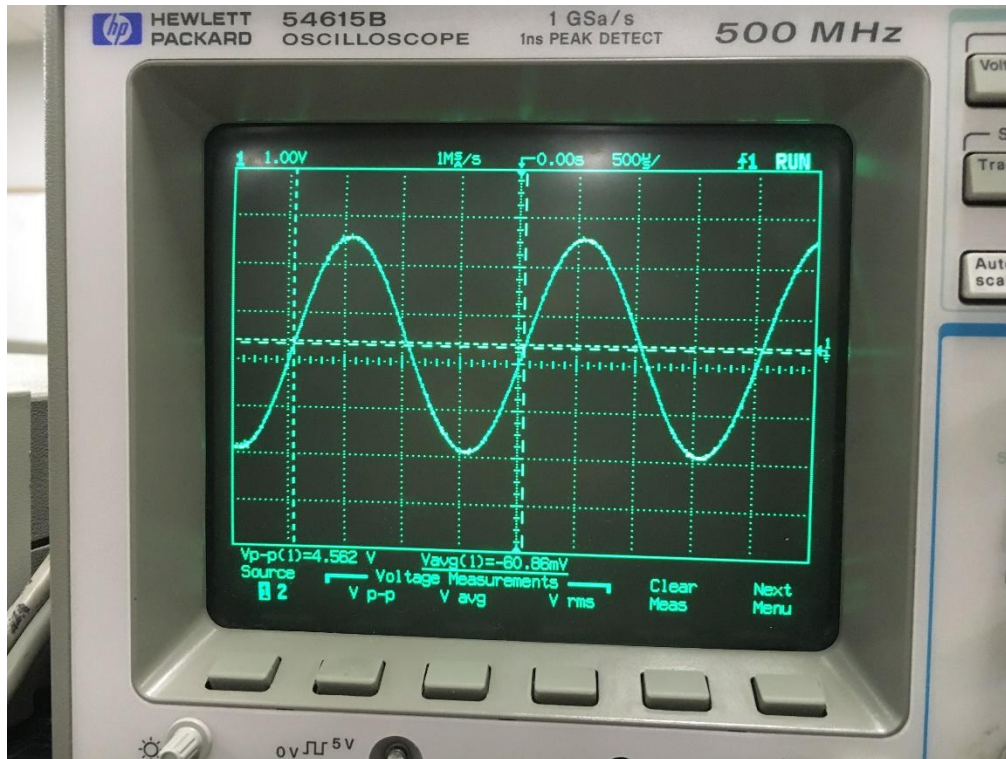


Fig 5: Input $V_{PP} = 0.1V$ and output $V_{PP} = 4.563$, giving the gain of 45.6

board, since that was the only difference the two boards had. We had high hopes with B20 since we were expecting a high amplification from it so we decided to go with it first. We were taking measurements step by step and as soon as we put all the LNAs in the board, the whole board shorted out. Since it wasn't all done the same day, we thought that maybe a random component went bad on the board. So, we replaced all the major components on the board and still the board was shorted. So we formed a hypothesis that the 20 dB LNA are either non-functional or not the best choice for the board since they were very hard to solder in the first place and we were not even sure that they were soldered right. We went ahead with B13 and it kept working. We decided to use this instead and see how it works in the lab conditions. Spectrum analyzer gave a very positive result and we were getting an amplification of 18 dBm at 5.8GHz (Fig 6)

while the 3.3V required to power the VCO to produce the 5.8GHz signal, was at 3.5V
(Fig 7)

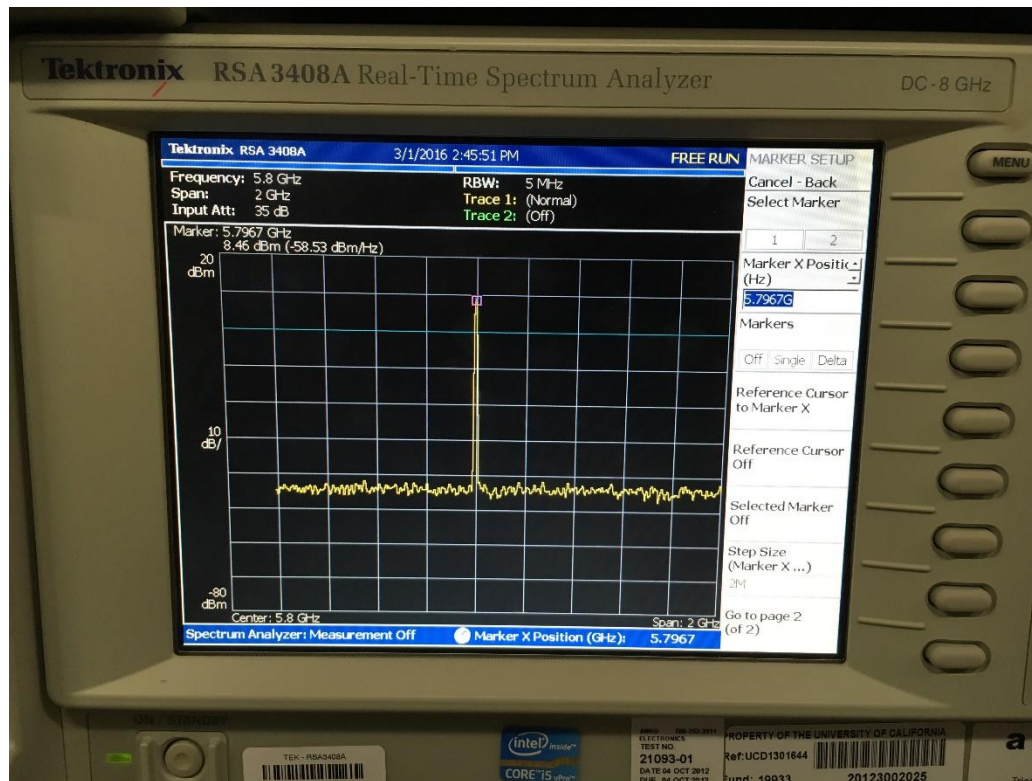


Fig 6: RF board measurements on Spectrum Analyzer

After finding some encouraging results from our baseband and RF boards, we decided to combine the boards together to see what kind of results it would produce. First, we tried to produce some results in the lab room by moving the metal sheet back and forth. We saw it producing some results on oscilloscope as the wave pattern seemed to be changing with every movement (Fig 8).

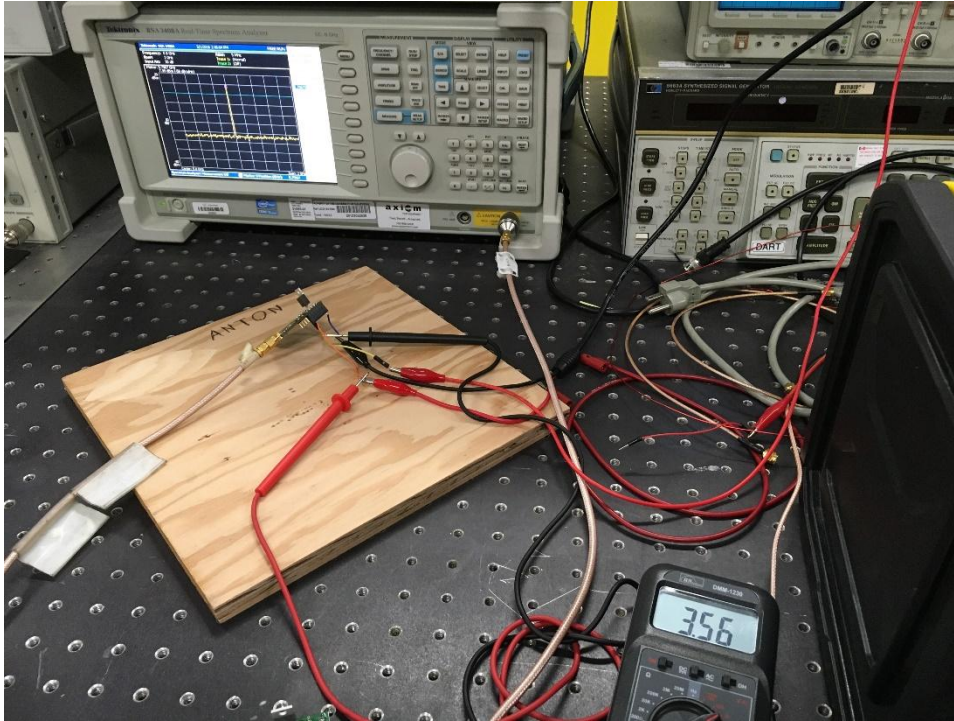


Fig 7: RF board during testing. We can see the voltage at VCO is 3.56V

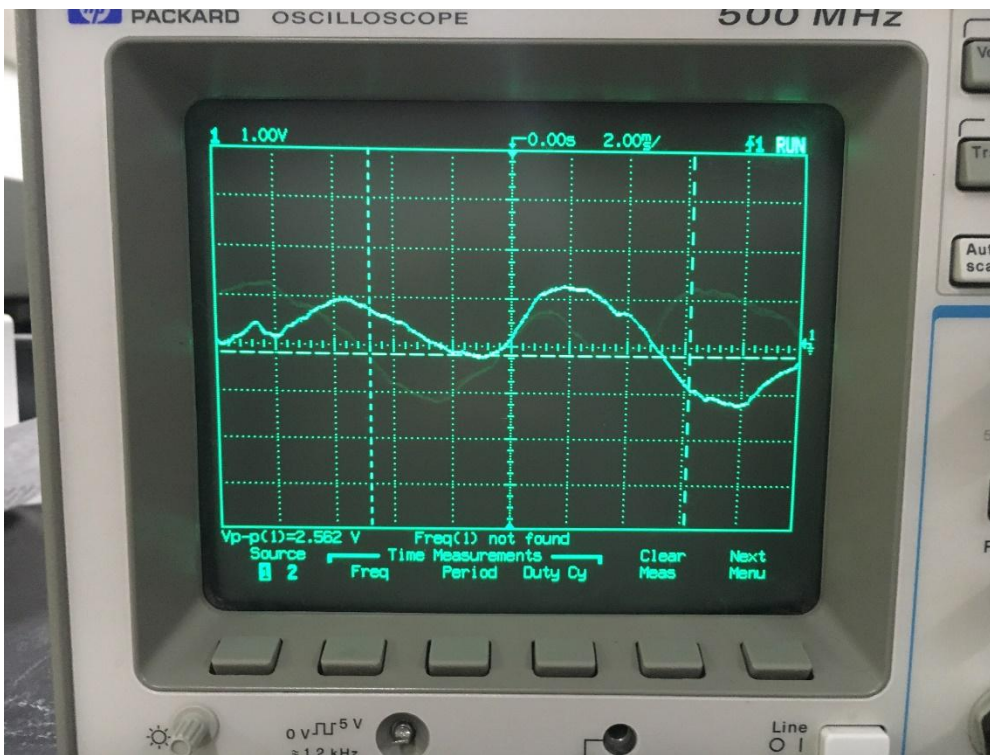


Fig 8: Wave patterns on the oscilloscope. The speed with which the patterns were changing, sometimes made it hard to have an exact value of frequency at that point.

5.8 GHz Patch Antenna Radar

03/03/2016: We went out for testing our radar for the first time in the field. For power source, we were using a portable car battery charger which gave a voltage of 12.5V. We added a fuse at the positive terminal of the battery charger to make sure the circuit stays safe in case the current gets really very high. Fortunately, the current value stayed fine and circuit seemed to be working but no optimal results were gained that day. As a matter of fact, the very first results gave no specific parameter and appeared just like noise in the circuit (Fig 9). It appeared like all the incoming signal was being diverted and nothing was being registered for the calculations but noise.

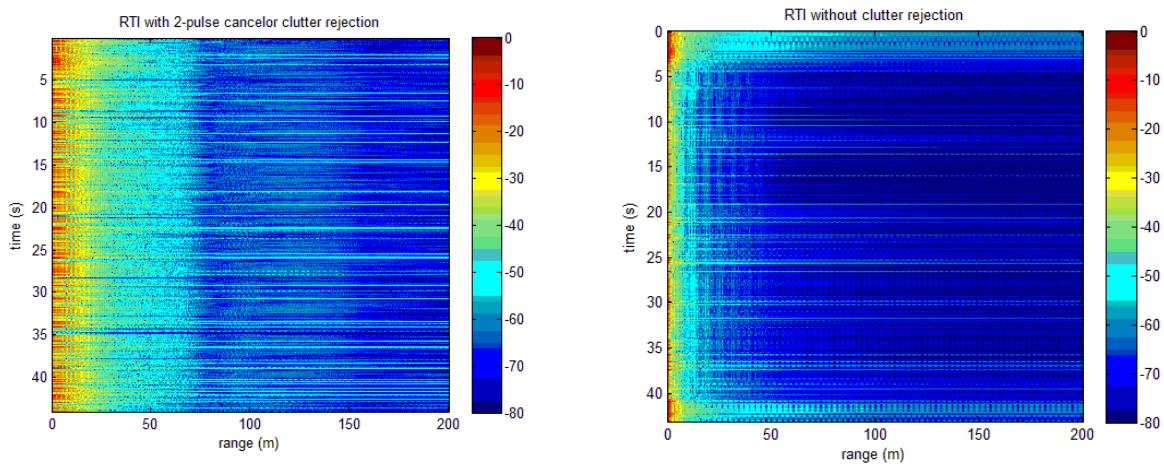


Fig 9: No encouraging results after the first test

03/08/2016: We thought about the top two layers of the antenna and that maybe they were reasons for diversion. We removed the layers to improve the directivity and took the circuit in the field and voila, we had a working radar (Fig 10). Although, the signal was very faint but still a curve in the graph could be seen, specifying a moving metal object. At this point, we had also added a heat sink to the VCO on our RF board since it was getting extremely hot and we were afraid it would burn out anytime.

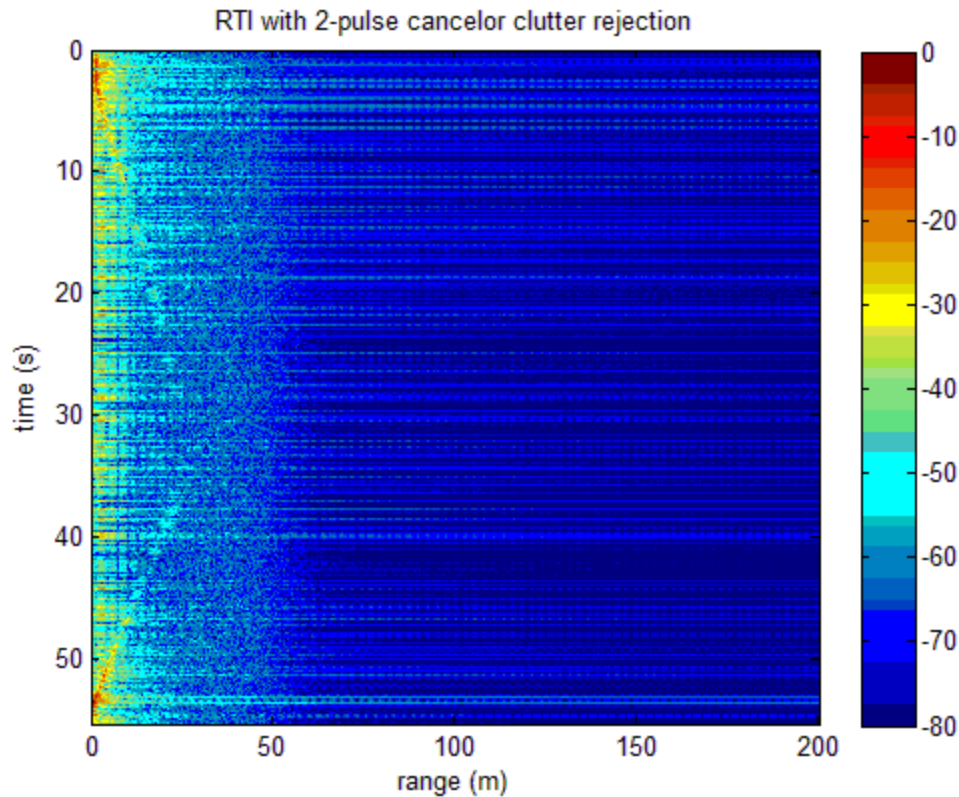


Fig 10: A faint curve showing that the radar was picking up some movement.

03/18/2016: Next time we came to the field to continue testing and see what needed to be improved, we had another baseband board ready to go with identical power amplification but with a limiter added after the low pass filter to limit the voltage entering the audio jack to make sure the audio jack stays safe. With the new baseband, radar gave absolutely zero results and all we saw was noise with a small speck which looked like a signal at the bottom left hand corner. We, then, tried to make the circuit work with the old baseband and still no result but noise. Our RF board was just not working anymore (Fig 11). After trying to swap some parts and failing to make the RF board work, we decided to work on the Lab 6 Coffee-Can radar as a backup plan in case we were not able to revive our RF board.

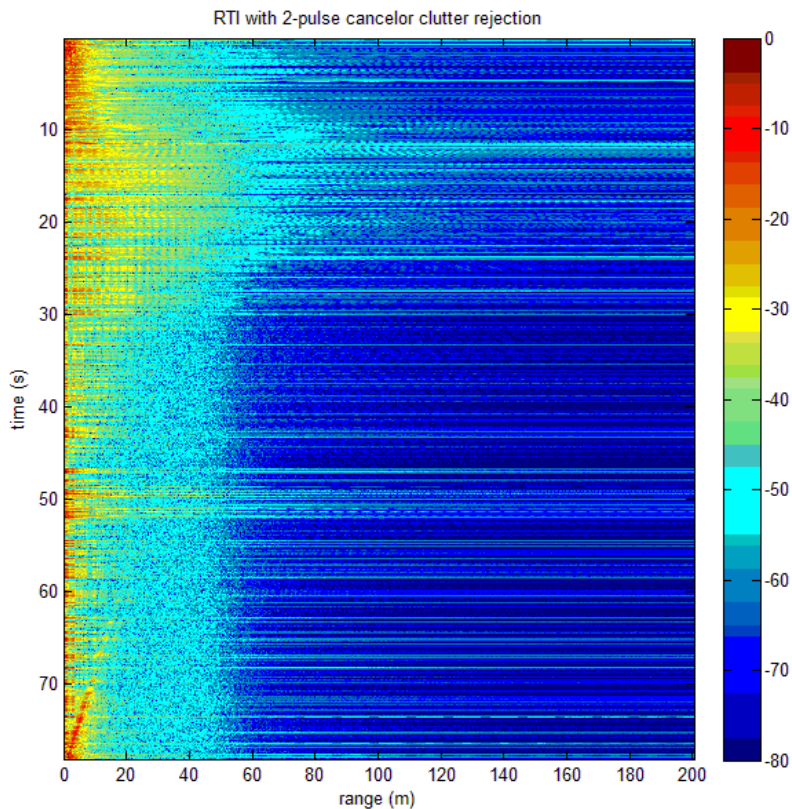


Fig 11: RF board stopped working for no apparent reasons.

Suggestions

In conclusion, I want to shed some light on the issues which can be proven useful for the future EEC134 students. First thing is, if unsure, build the circuit on the breadboard first to see the precision of the circuit. Second, the 20 dB LNAs from Mini-circuits are not a good option for the RF circuit. In any of our RF boards, when we tried to use that LNA, we got a short in the circuit. There was no way to check the connection of the LNA with the board either, since the pins are under the LNA and there is no way we would see the connection once the part was soldered.

Thirdly, even if you are told something is not available in the market, don't give up and try to find it anyways or may be try for an after-market alternative. We were told the XR2206 function generator was not available in the market. We did a little bit of research and in the end we were able to find an after-market version from china which worked just as great and saved us all the headache of working with Teensy and trying to produce the same exact results which we produced with a smaller component and a potentiometer. Fourth, RF results are lot better during a sunny day compared to a cloudy day and even worse for night. So, plan to do your testing on a good sunny day. Fifth, as I mentioned before, one gain stage for the baseband will work just as great as two gain stages and with lot less noise. You can always try to build it on the breadboard first if you want to test the accuracy of my statement. Sixth, for the limiter, it is best to use Zener diodes (consult Professor Momeni for more information on how these work to make a limiter). Seventh, do not but do not make 90 degree angles on transmission lines, since it will bring up the issue with return ratio and return loss. Lastly, always have a lot of test points, especially on the baseband board and especially after the gain stages, LPF, sync signal and limiter signal. It always helps you to find the problem at the most important parts of the circuit and helps you to take care of those problems without affecting any other part of circuit in any way.

Conclusion

This project covered the entire engineering process involved in designing and implementing a RF system from start to finish. We started out by researching design specifications used to meet the specific performance requirements. Once these system characteristics were well defined, the implementation process of component selection was undertaken. This led to the design of schematic CAD drawings and printed circuit board layouts which were sent out for fabrication. The purchasing process was taken care of to insure the parts arrived when the PCBs were received from fabrication. Next the PCB assembly process required extensively precise soldering work to insure proper connection of components without any shorts. We finished with fine tuning, modifying and field testing of the complete radar.

Overall the radar performed reasonably well. During the testing phase of the project, our radar was able to detect a 0.3 meter squared metal target at distances of 25 meters in the field. More time spent on fine tuning distance measurements would have been greatly helpful in reducing noise and distortion in our readings to achieving the 50 meter range mark. In conclusion this project provides the engineering skills required to take on and overcome the challenges presented in RF system design.

Appendix

MatLab Code:

```
%MIT IAP Radar Course 2011
%Resource: Build a Small Radar System Capable of Sensing Range, Doppler,
%and Synthetic Aperture Radar Imaging
%
%Gregory L. Charvat

%Process Range vs. Time Intensity (RTI) plot

%NOTE: set up-ramp sweep from 2-3.2V to stay within ISM band
%change fstart and fstop below when in ISM band

clear all;
close all;

%read the raw data .wave file here
[Y,FS,NBITS] = wavread('running_outside_20ms.wav');

%constants
c = 3E8; %(m/s) speed of light

%radar parameters
Tp = 20E-3; %(s) pulse time
N = Tp*FS; %# of samples per pulse
fstart = 2260E6; %(Hz) LFM start frequency for example
fstop = 2590E6; %(Hz) LFM stop frequency for example
%fstart = 2402E6; %(Hz) LFM start frequency for ISM band
%fstop = 2495E6; %(Hz) LFM stop frequency for ISM band
BW = fstop-fstart; %(Hz) transmit bandwidth
f = linspace(fstart, fstop, N/2); %instantaneous transmit frequency

%range resolution
rr = c/(2*BW);
max_range = rr*N/2;

%the input appears to be inverted
trig = -1*Y(:,1);
s = -1*Y(:,2);
clear Y;
```

```

%parse the data here by triggering off rising edge of sync pulse
count = 0;
thresh = 0;
start = (trig > thresh);
for ii = 100:(size(start,1)-N)
    if start(ii) == 1 & mean(start(ii-11:ii-1)) == 0
        %start2(ii) = 1;
        count = count + 1;
        sif(count,:) = s(ii:ii+N-1);
        time(count) = ii*1/FS;
    end
end
%check to see if triggering works
% plot(trig,'.b');
% hold on;si
% plot(start2,'.r');
% hold off;
% grid on;

%subtract the average
ave = mean(sif,1);
for ii = 1:size(sif,1);
    sif(ii,:) = sif(ii,:) - ave;
end

zpad = 8*N/2;

%RTI plot
figure(10);
v = dbv(iff(sif,zpad,2));
S = v(:,1:size(v,2)/2);
m = max(max(v));
imagesc(linspace(0,max_range,zpad),time,S-m,[-80, 0]);
colorbar;
ylabel('time (s)');
xlabel('range (m)');
title('RTI without clutter rejection');

%2 pulse cancelor RTI plot
figure(20);
sif2 = sif(2:size(sif,1),:)-sif(1:size(sif,1)-1,:);
v = ifft(sif2,zpad,2);
S=v;
R = linspace(0,max_range,zpad);
for ii = 1:size(S,1)
    %S(ii,:) = S(ii,:).*R.^(3/2); %Optional: magnitude scale to range
end
S = dbv(S(:,1:size(v,2)/2));
m = max(max(S));
imagesc(R,time,S-m,[-80, 0]);
colorbar;
ylabel('time (s)');
xlabel('range (m)');
title('RTI with 2-pulse cancelor clutter rejection');

% %2 pulse mag only cancelor

```

```

% figure(30);
% clear v;
% for ii = 1:size(sif,1)-1
%     v1 = abs(ifft(sif(ii,:),zpad));
%     v2 = abs(ifft(sif(ii+1,:),zpad));
%     v(ii,:) = v2-v1;
% end
% S=v;
% R = linspace(0,max_range,zpad);
% for ii = 1:size(S,1)
%     S(ii,:) = S(ii,).*R.^(3/2); %Optional: magnitude scale to range
% end
% S = dbv(S(:,1:size(v,2)/2));
% m = max(max(S));
% imagesc(R,time,S-m,[-20, 0]);
% colorbar;
% ylabel('time (s)');
% xlabel('range (m)');
% title('RTI with 2-pulse mag only cancelor clutter rejection');

```

Bill of Materials:

Description	Quantity	Unit Price	Extended Price
XR2206CP Function Generator	3	7.95	23.85
Ripafire 5.8 GHz 4 Patch Array Antenna	2	11.49	22.98
LM317 Adjustable Voltage Regulator	4	0	0
SMA Connector	4	0	0
1mF Capacitor (size: 0603)	5	0	0
10mF Capacitor (size: 0603)	5	0	0
22pF Capacitor (size: 0603)	5	0	0
0.1mF Capacitor (size: 0603)	5	0	0
10,000pF Capacitor (size: 0603)	5	0	0
2.7mF Capacitor (size: 0603)	5	0	0
10mF Capacitor (size: 0603)	5	0	0
10k Ohm Resistor (size 0603)	5	0	0
220 Ohm Resistor (size 0603)	5	0	0
1k Ohm Resistor (size 0603)	5	0	0
100 Ohm Resistor (size 0603)	5	0	0
Zener Diode	4	0	0
2M Ohm Potentiometer	4	0	0
PDIP8 Socket	4	0	0
PDIP16 Socket	4	0	0
Texas Instruments TL972IP Amplifier	4	0.91	3.64
Conn Header 2Pos	5	0.16	0.80
LT1009CZ 2.5V Regulator	4	2.61	10.44
Analog Devices HMC218BMS8GE Mixer	4	6.76	27.04
Analog Devices HMC431LP4ETR (VCO)	4	19.96	79.84
Analog Devices HMC320MS8GE (LNA)	12	4.58	54.96
LM2937ET 3.3V Regulator	5	1.53	7.65
50K Ohm Potentiometer	2	2.41	4.82
20K Ohm Potentiometer	4	2.41	9.64
2K Ohm Potentiometer	4	2.41	9.64
5.1K Ohm Resistor (size: 0603)	10	0.013	0.13
3.6K Ohm Resistor (size: 0603)	10	0.011	0.11
Conn Header 5Pos	10	0.385	3.85
6.98 Ohm Resistor (size: 0603)	20	0.081	1.62
10pF Capacitor (size: 0603)	10	0.03	0.30

18nH Inductor (size: 0603)	10	0.064	0.64
39nH Inductor (size: 0603)	10	0.064	0.64
Heatsink – TO-220	6	0.21	1.26
		Total	\$263.85
Mini-Circuits SCN-2-65+ Power Splitter	8	Sampled	
Maxim Integrated MAX291CPA+ (LPF)	4	Sampled	

Acknowledgements

We would like to thank Professor Xiaoguang Liu for providing the opportunity for us to participate in such a challenge design project.

We would like to thank Mini-Circuits for providing samples of RF components.

We would like to thank Maxim Integrated for providing samples of their active low pass filter.

We would like to thank Hao Wang for providing technical help and support in the lab.